

## Problem Set 6 - LV 141.A55 QISS - 2.5.2016

**1. SQUID with unequal junctions** Consider a SQUID with two unequal junctions ( $I_l$  and  $I_r$ ). Calculate the switching current, i.e. maximum super current.

**2. RCSJ model - pendulum**

Compare the resistively and capacitively shunted junction (RCSJ) model of a Josephson junction with model of a pendulum including friction. Identify the quantities like torque, angular momentum and relate them to the RCSJ parameters.

**3. RCSJ model - overdamped**

Solve the RCSJ model in the strongly over damped limit, i.e.  $Q \ll 1$ . Calculate the voltage versus current relation.